

Overview of Logic Design

CS2011: Introduction to Computer Systems
Lecture 16 (4.2)

Overview of Logic Design


Fundamental Hardware Requirements

- **Communication**
 - How to get values from one place to another
- **Computation**
- **Storage**

Bits are Our Friends


- **Everything expressed in terms of values 0 and 1**
- **Communication**
 - Low or high voltage on wire
- **Computation**
 - Compute Boolean functions
- **Storage**
 - Store bits of information

Digital Signals

 


- Use voltage thresholds to extract discrete values from continuous **signal**
- Simplest version: **1-bit signal**
 - Either high range (1) or low range (0)
 - With guard range between them
- Not strongly affected by noise or low quality circuit elements
 - Can make circuits simple, small, and fast





Computing with Logic Gates

 

 
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
 - With some, small **delay**



Computing with Logic Gates

    


Combinational Circuits

 

Acyclic Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

Bit Equality

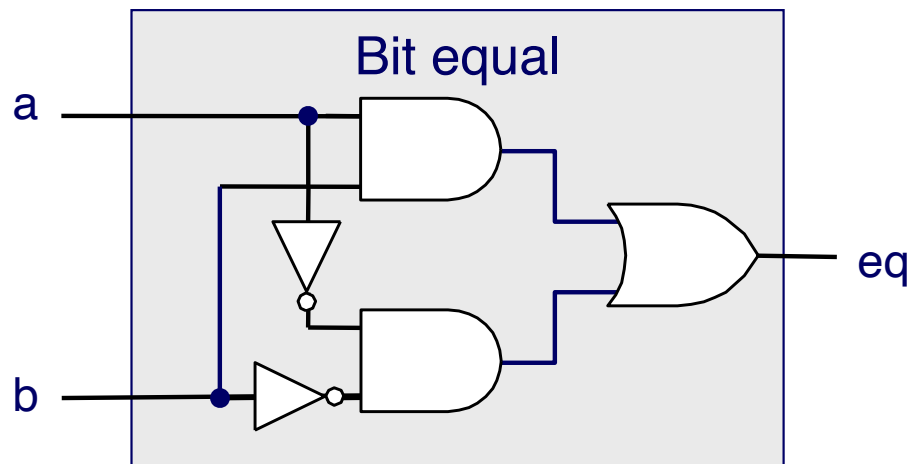

HCL Expression


```
bool eq = (a&&b) || (!a&&!b)
```

- Generate 1 if a and b are equal


Hardware Control Language (HCL)

- Very simple hardware description language
 - Boolean operations have syntax similar to C logical operations
- We'll use it to describe control logic for processors

Word Equality

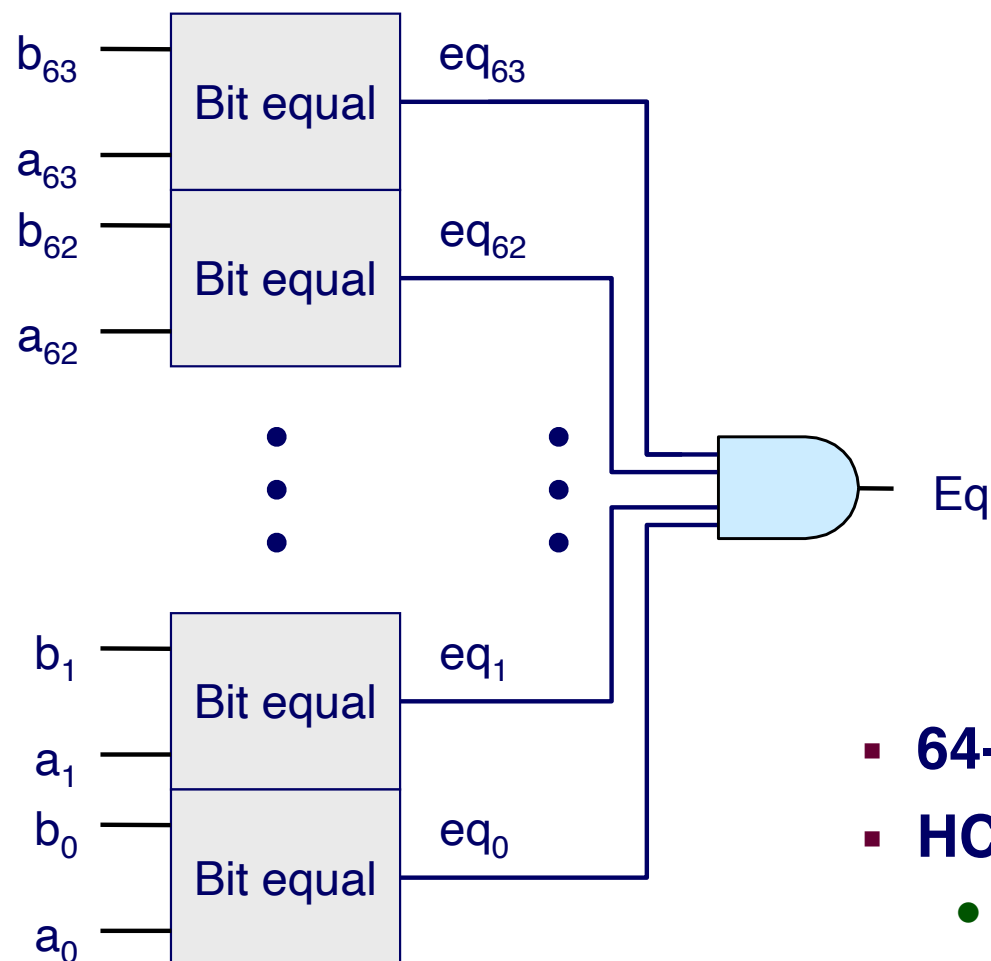

Word-Level Representation

 


HCL Representation

`bool Eq = (A == B)`

- 64-bit word size
- HCL representation
 - Equality operation
 - Generates Boolean value (dotted line is 1 bit)

Bit Xor

 

HCL Expression


```
bool xor = (!a&&b) || (a&&!b)
```

- Generate 1 if a and b are not equal
- Output is complement of the bit equality value

```
xor = !eq
```


Word Equality using Bit Xor

Word-Level Representation

 


HCL Representation

`bool Eq = (A == B)`

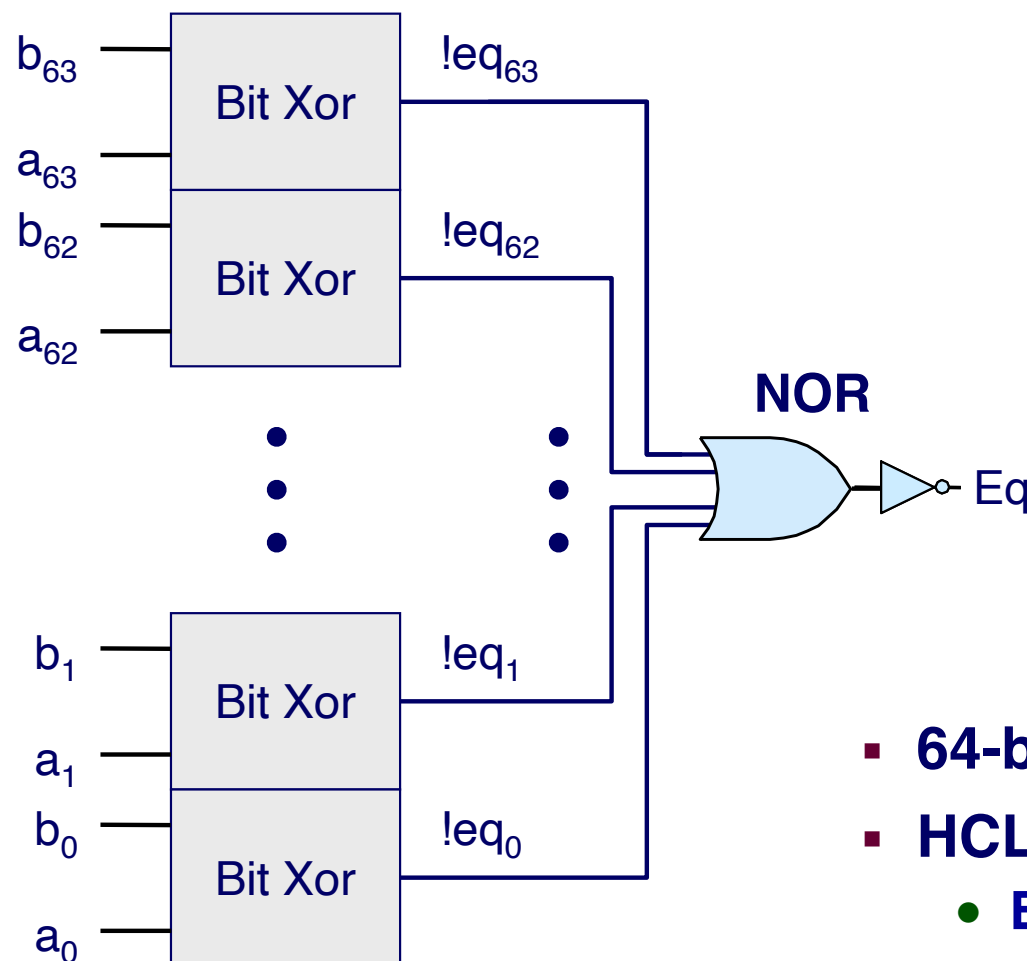

- 64-bit word size
- HCL representation
 - Equality operation
 - Generates Boolean value (dotted line is 1 bit)

Bit-Level Multiplexor

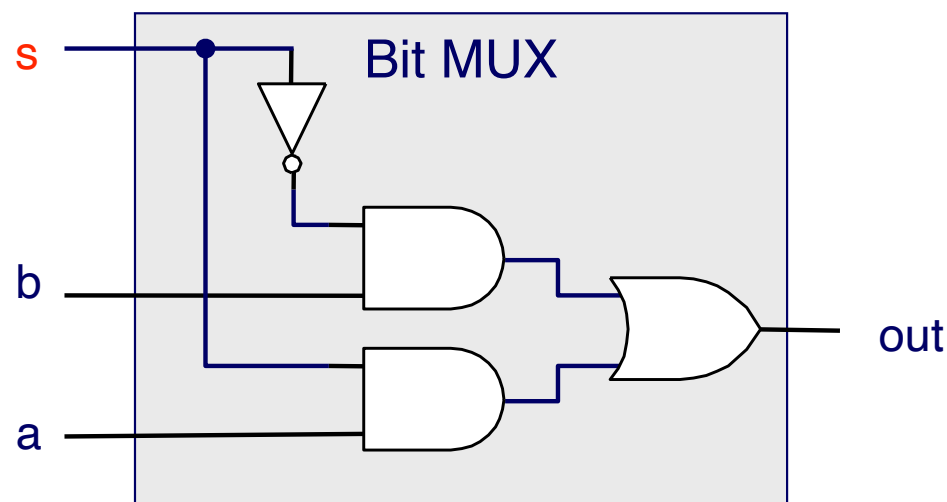


HCL Expression


```
bool out = (s&&a) || (!s&&b)
```

- **Control signal **s****
- **Data signals **a** and **b****
- **Output **a** when **s=1**, **b** when **s=0****

Word Multiplexor

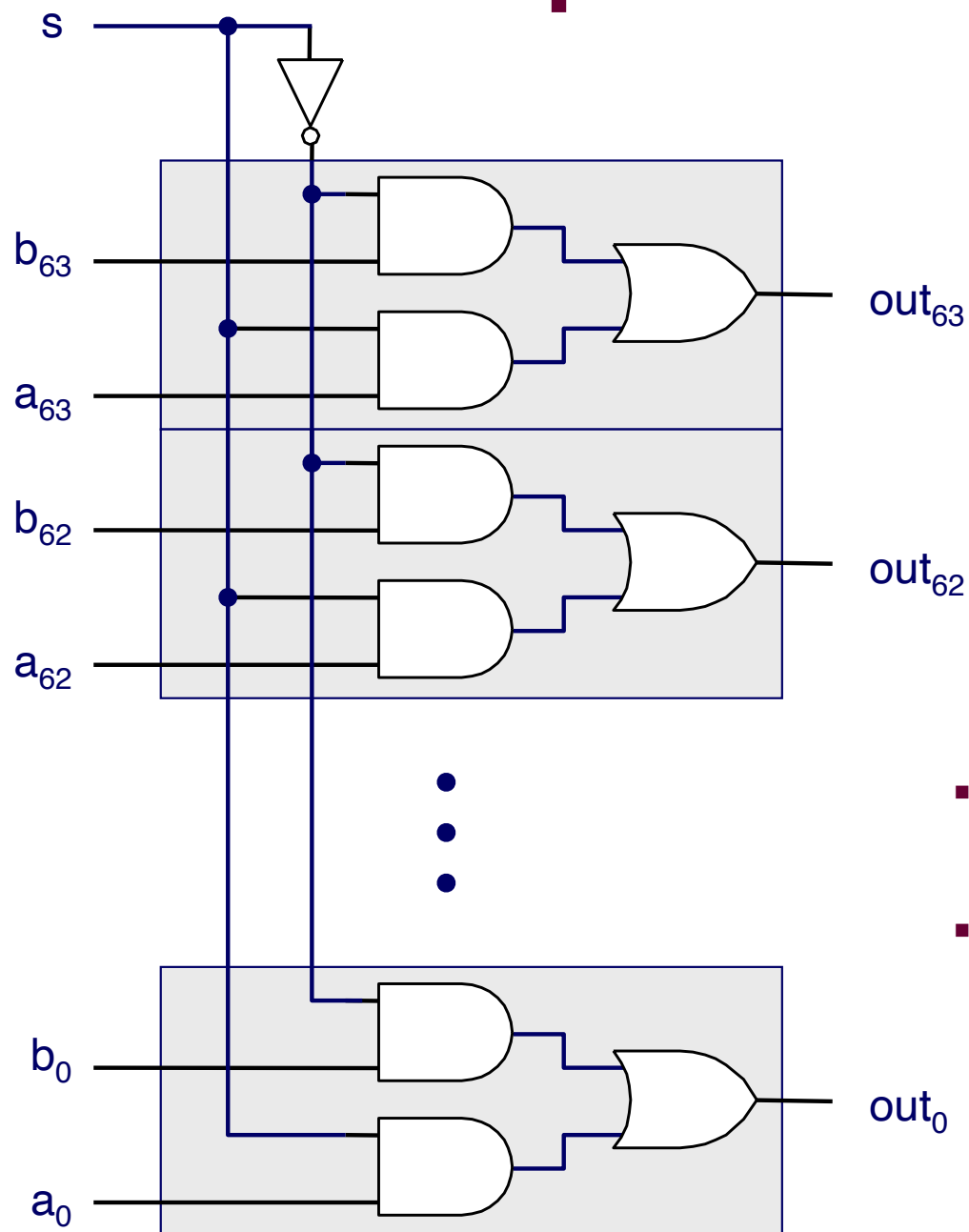

Word-Level Representation

 


HCL Representation

```
int Out = [
    s : A;
    1 : B;
];
```

- Select input word A or B depending on control signal s
- HCL representation
 - Case expression
 - Series of test : value pairs
 - Output value for first successful test

HCL Word-Level Examples


Minimum of 3 Words

 

```
int Min3 = [
    A < B && A < C : A;
    B < A && B < C : B;
    1               : C;
];
```

- Find minimum of three input words
- HCL case expression
- Final case guarantees match


4-Way Multiplexor

 

```
int Out4 = [
    !s1&&!s0: D0; #00
    !s1      : D1; #01
    !s0      : D2; #10
    1        : D3; #11
];
```

- Select one of 4 inputs based on two control bits
- HCL case expression
- Simplify tests by assuming sequential matching


Arithmetic Logic Unit

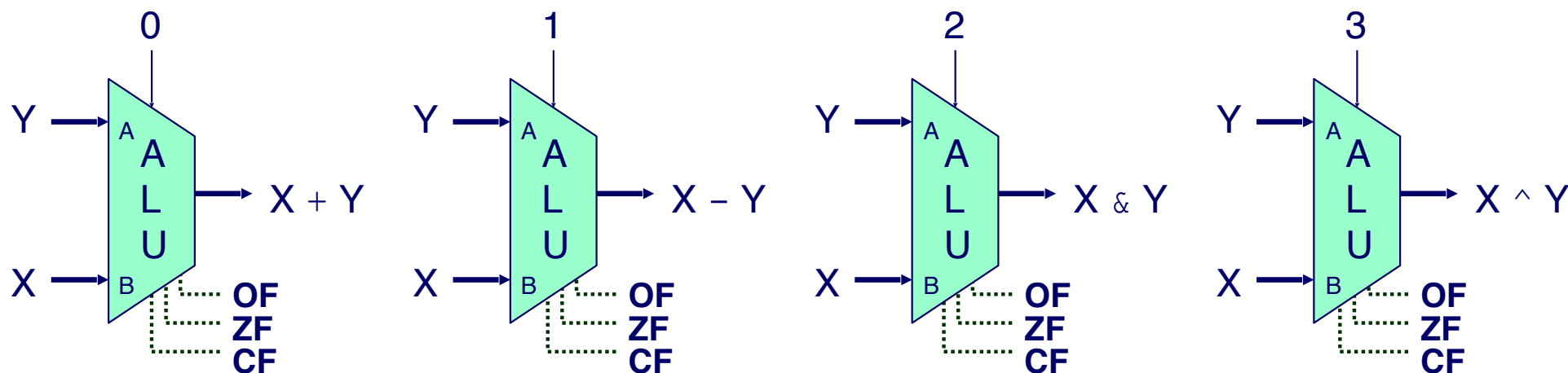

- **Combinational logic**
 - Continuously responding to inputs
- **Control signal selects function computed**
 - Corresponding to 4 arithmetic/logical operations in Y86-64
- **Also computes values for condition codes**

{	addq	6	0
	subq	6	1
	andq	6	2
	xorq	6	3

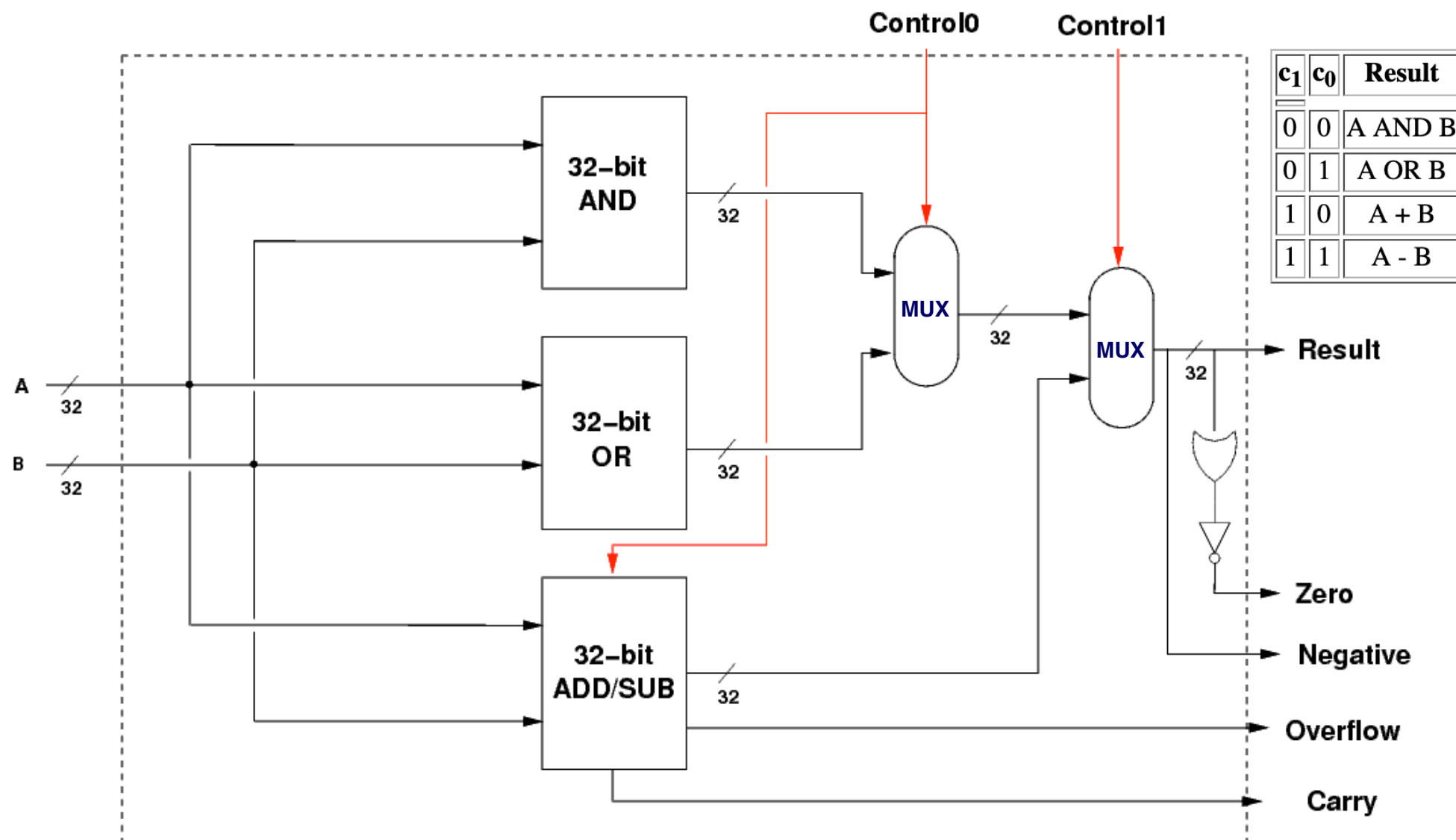
Simple Arithmetic Logic Unit (Example Implementation) - AND/OR/ADD/SUB





Source: <http://www.csc.villanova.edu/~mdamian/Past/csc2400fa13/assign/ALU.html>

Storing 1 Bit

Bistable Element

 


$q = 0 \text{ or } 1$

 
 


Storing 1 Bit

Bistable Element

 


$q = 0 \text{ or } 1$

  


Storing 1 Bit


Bistable Element

 



$q = 0 \text{ or } 1$

 

Stable 0

 


Physical Analogy

 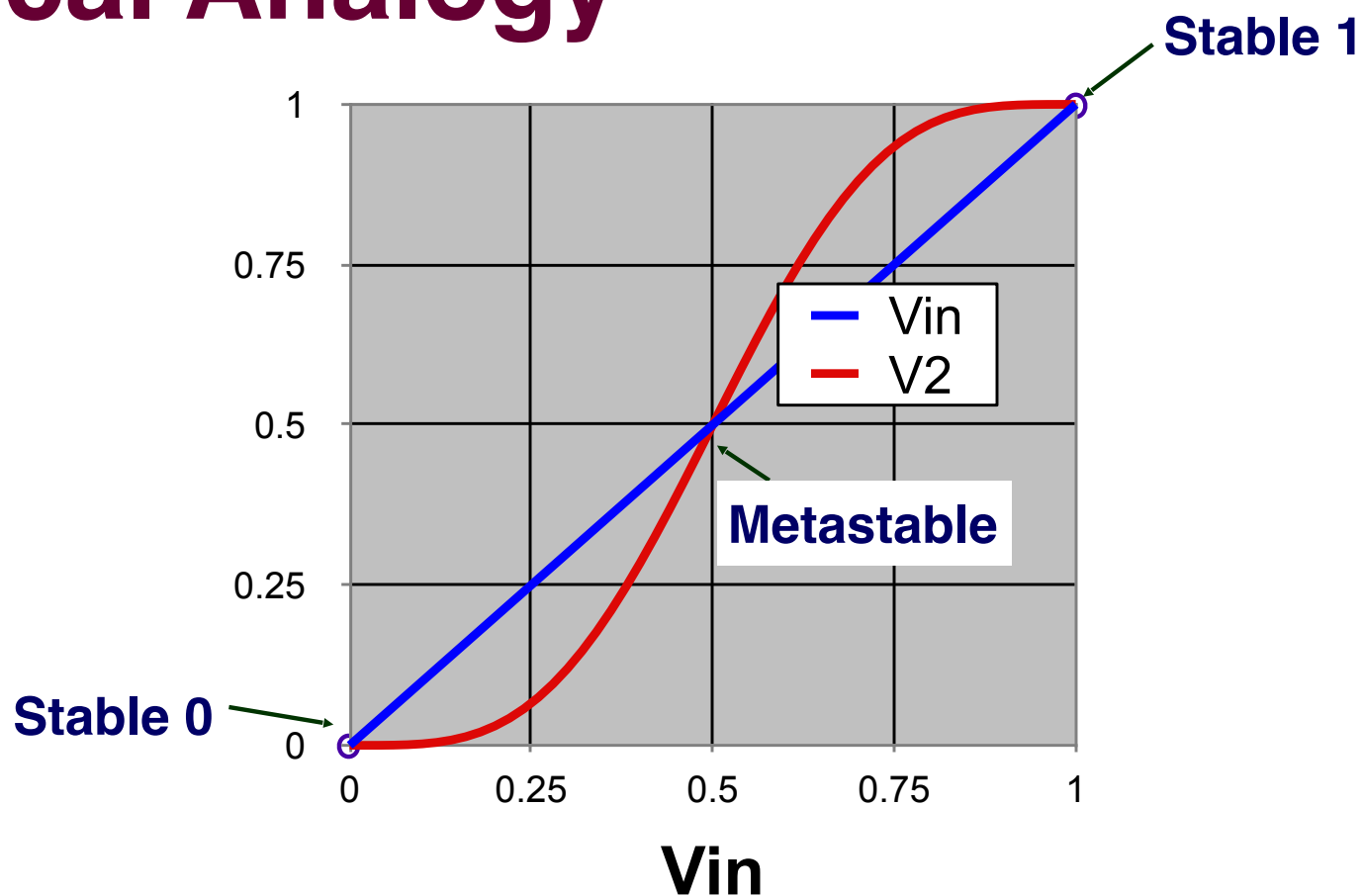


S-R Latch

Bistable Element

 


$q = 0 \text{ or } 1$


S-R Latch

 


Resetting

 


Setting

 


Storing

 


Transparent 1-Bit D-Latch

 

Latching

 


Storing

 


Transparent 1-Bit D-Latch

Latching


 


Changing D

 



- When in latching mode, combinational propagation from D to $Q+$ and $Q-$
- Value latched depends on value of D as C falls

Edge-Triggered Latch (D Flip-Flop)

 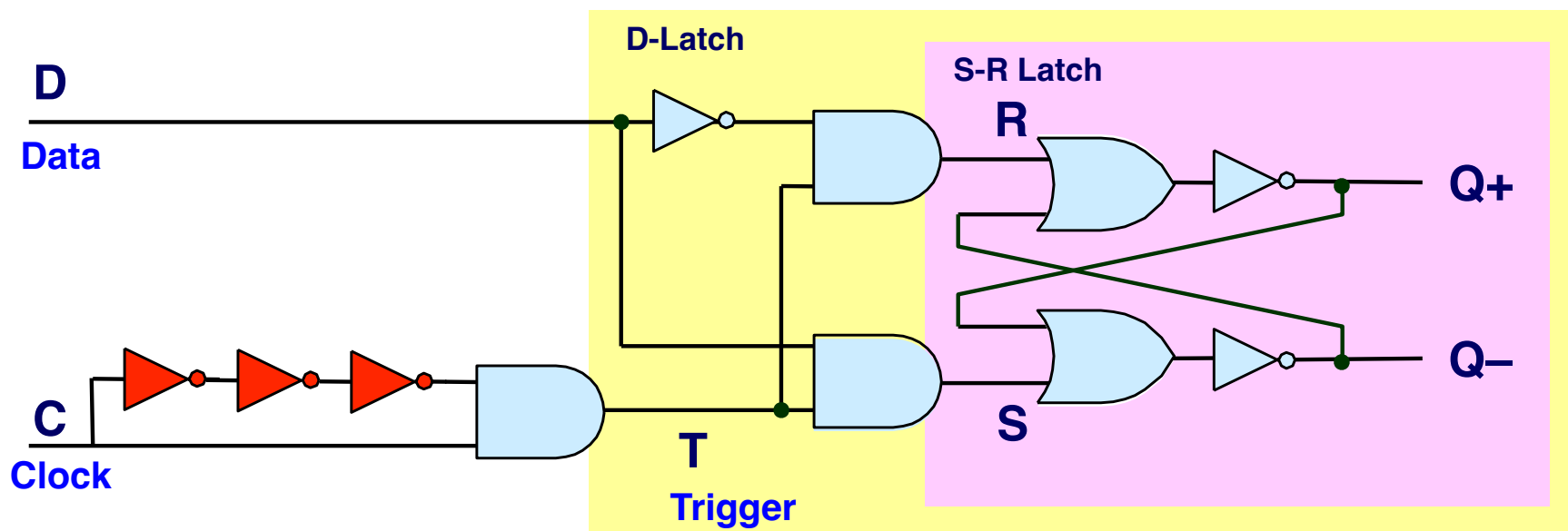


- Adding **three inverters** help us delay the Clock change and get a PULSE/ Trigger only on the rising edge of the clock
- Only in **latching mode for brief period**
 - Rising clock edge
- Value latched depends on data as clock rises
- Output remains stable at all other times

Hardware Registers

 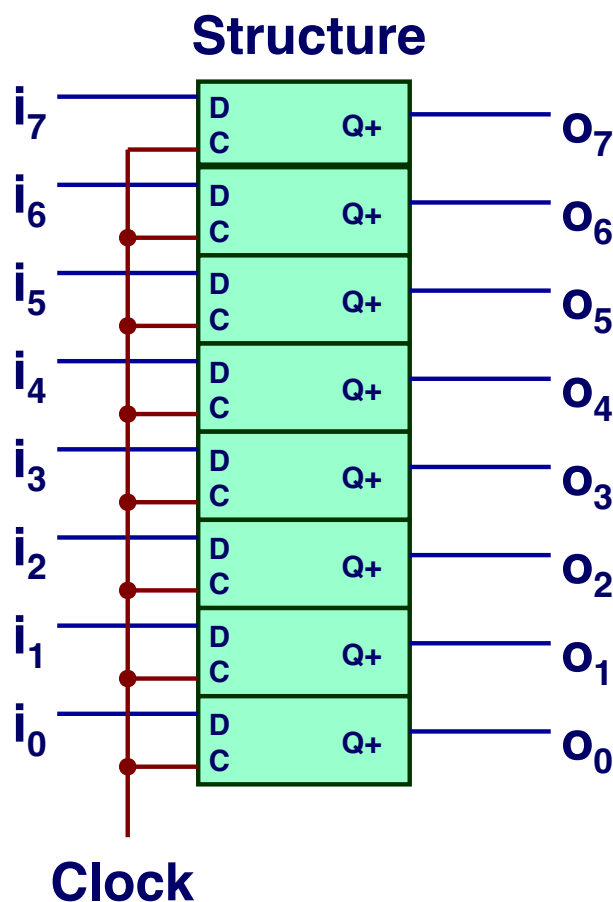


- **Stores individual word of data**
 - Different from *program registers* seen in assembly code
- **Collection of edge-triggered latches (D Flip-Flops)**
- **Loads input on rising edge of clock**

Register Operation

 

- **Stores data bits**
- **For most of time acts as barrier between input and output**
- **As clock rises, loads input**

State Machine Example

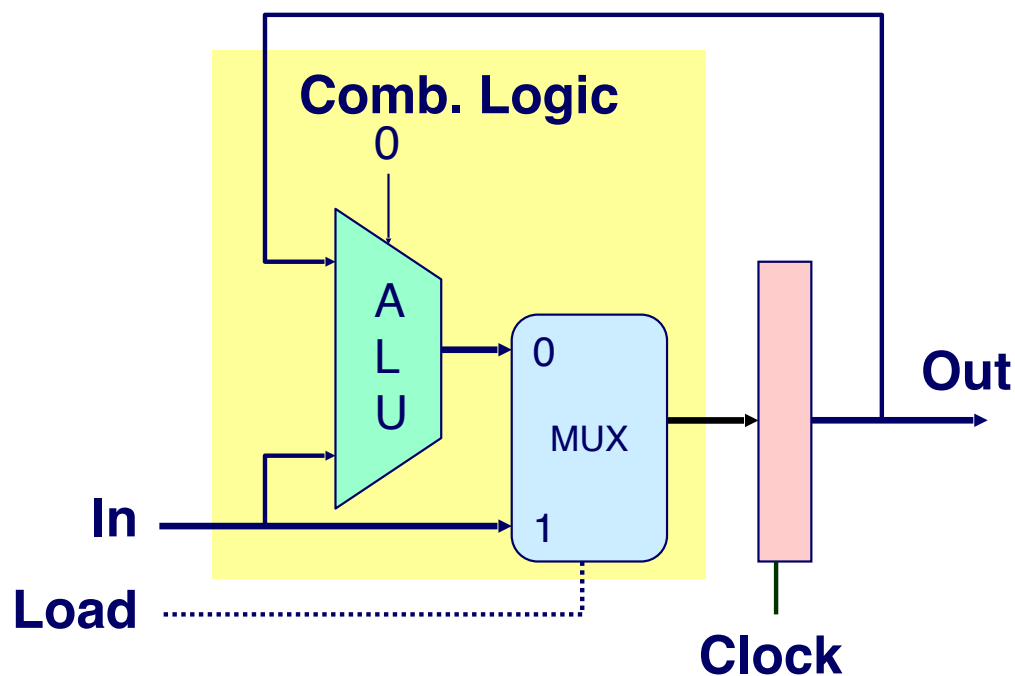

- Accumulator circuit
- Load or accumulate on each cycle

